



DHARMSINH DESAI UNIVERSITY, NADIAD
FACULTY OF TECHNOLOGY
B.TECH - IT - Semester - III
SUBJECT: (IT 301) Design of Digital Circuits

Examination : Third Sessional
Date : 11/10/2014
Time : 9:30 to 10:45

Seat No. :
Day : Saturday
Max. Marks : 36

INSTRUCTIONS:

1. Figures to the right indicate maximum marks for that question.
2. The symbols used carry their usual meanings.
3. Assume suitable data, if required & mention them clearly.
4. Draw neat sketches wherever necessary.

Q.1 Do as directed. [12]

- (a) Obtain Characteristic Table and Excitation table of RS flip-flop. [2]
- (b) What is the difference between serial and parallel transfer? What type of register is used in each case? [2]
- (c) The memory unit has capacity of 8192 words of 32 bits/word. What is the length of a memory address (input bits)? [2]
- (d) What are decade counters? Show the block diagram of a BCD counter which counts from 0 to 999. [3]
- (e) Explain the working of Ring-counter with logic diagram. [3]

Q.2 Attempt following questions. [12]

- (a) Answer the following: [6]
 - (I) Draw and explain basic memory cell used in Random Access Memory. [4]
 - (II) Define the following term: (1) Bit Time (2) Word Time [2]
- (b) Design a counter with the following binary sequence: **0,1,5,7,6,4** and repeat. Use T flip-flops. Draw the logic diagram. [6]

OR

- (b) Design a sequential circuit described by the following state equations. Use JK flip-flops. [6]
 $A(t+1) = xAB + yA'C + xy$
 $B(t+1) = xAC + y'BC'$
 $C(t+1) = x'B + yAB'$

Q.3 Attempt following questions [12]

- (a) Reduce the no of states in the following state table **fig-1** & tabulate the reduced state table. State no of flip flop required before and after reduction. [4]
- (b) A sequential circuit has the flip-flops (**X & Y**), two inputs (**a & b**), and one output (**c**). The flip-flop input function and the circuit output function are as follow: [8]
 $JX = aY + b'Y'$ $JY = aX'$ $c = abX + a'b'Y$
 $KX = ab'Y'$ $KY = ab' + X$

Obtain the **state table** and **state diagram**.

OR

Q.3 Attempt following questions [12]

- (a) Construct a mod 08-counter using MSI circuit. Give two alternatives [4]
- (b) Design a sequential circuit whose state table is given below (**fig-2**) using a 2-bit register and combinational gates. (draw the logic diagram). [8]

Present state	Next state		Output	
	X=0	X=1	X=0	X=1
a	f	b	0	0
b	d	c	0	0
c	f	e	0	0
d	g	a	1	0
e	d	c	0	0
f	f	b	1	1
g	g	h	0	1
h	g	a	1	0

(Fig-1)

Present State		Input	Next State	
A	B	x	A	B
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	1	1
1	1	0	1	0
1	1	1	0	1

(Fig-2)