



**DHARMSINH DESAI UNIVERSITY, NADIAD**  
**FACULTY OF TECHNOLOGY**  
**B.TECH - IT - Semester - III**  
**SUBJECT: (IT 301) Design of Digital Circuits**

**Examination : Third Sessional**  
**Date : 15/10/2016**  
**Time : 11:00 to 12:15**

**Seat No. :**  
**Day : Saturday**  
**Max. Marks : 36**

**INSTRUCTIONS:**

1. Figures to the right indicate maximum marks for that question.
2. The symbols used carry their usual meanings.
3. Assume suitable data, if required & mention them clearly.
4. Draw neat sketches wherever necessary.

**Q.1 Do as directed. [12]**

- (a) Convert S-R flip-flop to J-K flip-flop. [2]
- (b) What are decade counters? Show block diagram of BCD counter which counts 0 to 9999. [2]
- (c) "Asynchronous counters are faster than synchronous counters". State T/F with justification. [1]
- (d) Why Flip Flop is called a single-bit register? [1]
- (e) Construct a mod 11-counter using MSI circuit. Give two alternatives. [3]
- (f) Design a 3-bit Ripple counter using D Flip-flop. [3]

**Q.2 Attempt following questions. [12]**

- (a) Reduce the state of state table given in **Table-1** below. Also provide the binary state assignment to reduce states. [6]
- (b) Design a Johnson counter with attached AND gates require for outputs to generate 12 timing signals. [6]

**OR**

- (b) Design a circuit which generates Timing signals (8-timing sequence) for parallel mode of operation. Also represent the sequence of 8 timing signals. [6]

**Q.3 Attempt following questions [12]**

- (a) Using MSI of 4-bit counter with parallel load, construct a binary counter that counts from 0 to binary 64. [2]
- (b) Design a serial adder using sequential logic procedure.(use T Flip-flop) [4]
- (c) Design a sequential circuit whose state diagram is shown in **Figure-A** below. The type of flip-flop to be use is RS. [6]


**OR**

**Q.3 Attempt following questions [12]**

- (a) Obtain characteristic Table and Excitation table of RS flip-flop. [2]
- (b) Draw and explain basic memory cell used in Random Access Memory. [4]
- (c) Design a counter with the following binary sequence: 0,3,4,2,7 and repeat. Use JK flip-flops. [6]

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
A	B	C	0	0
B	D	E	0	0
C	F	G	0	0
D	H	I	0	0
E	J	K	0	0
F	L	M	0	0
G	N	P	0	0
H	A	A	0	0
I	A	A	0	0
J	A	A	0	1
K	A	A	0	0
L	A	A	0	1
M	A	A	0	0
N	A	A	0	0
P	A	A	0	0

**Table - 1**

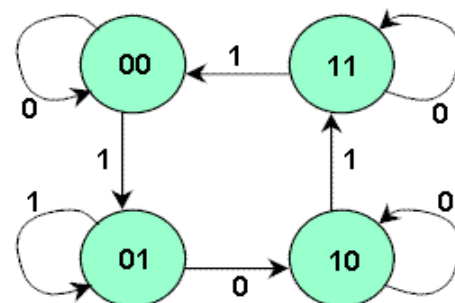

**Figure-A**