



DHARMSINH DESAI UNIVERSITY, NADIAD
FACULTY OF TECHNOLOGY
B.TECH - Semester - III
SUBJECT: (IT 301) Design of Digital Circuits

Examination : Second Sessional
Date : 05/09/2014
Time : 9:30 to 10:45

Seat No. :
Day : Friday
Max. Marks : 36

INSTRUCTIONS:

1. Figures to the right indicate maximum marks for that question.
 2. The symbols used carry their usual meanings.
 3. Assume suitable data, if required & mention them clearly.
 4. Draw neat sketches wherever necessary.
-

- Q.1 Do as directed. [12]**
- (a) How many don't care inputs are there in a BCD adder? Show your calculations. [2]
 - (b) PLA consists of 8 inputs, 8 product terms and 8 sum terms. It will have total ____ number of programmable links. Show your calculations. [2]
 - (c) How do look ahead carry adder speed up the addition process? [2]
 - (d) Determine ROM size to implement 6 Boolean functions of 6 variables each. [2]
 - (e) What is Priority Encoder. Explain giving example. [2]
 - (f) Define: Propagation Delay and Power Dissipation [2]
- Q.2 Attempt following questions. [12]**
- (a) Determine the equations: greater than, less than and equal to for 4-bit magnitude comparator. [3]
 - (b) Implement the following function using only NAND gates.
 $F = A(B+CD) + BC'$ [3]
 - (c) Obtain sum of minterms (in canonical form) of output functions for a combinational circuit that converts a decimal digit from the 8,4,-2,-1 code to BCD code and implement it with decoder and NAND gates [6]
- OR**
- (c) Obtain sum of minterms (in canonical form) of output function for a 4 bit odd parity checker and implement it with a multiplexer. Variables given are A,B,C,C' and D [6]
- Q.3 Attempt following questions [12]**
- (a) Show the derivation table and block diagram of a BCD Adder. [4]
 - (b) List the PLA program table for BCD to Excess-3 coder convertor circuit. [8]
- OR**
- Q.3 Attempt following questions [12]**
- (a) Design a combinational circuit using ROM. The circuit accepts 4-bit binary number and generates 4-bit reflected code at the output [4]
 - (b) List the PLA program table for BCD to 9's complement code convertor circuit. [8]