



DHARMSINH DESAI UNIVERSITY, NADIAD
FACULTY OF TECHNOLOGY
B.TECH - IT - Semester - III
SUBJECT: (IT 301) Design of Digital Circuits

Examination : Block-Regular
Date : 21/10/2016
Time : 3:00 to 04:15

Seat No. :
Day : Friday
Max. Marks : 36

INSTRUCTIONS:

1. Figures to the right indicate maximum marks for that question.
2. The symbols used carry their usual meanings.
3. Assume suitable data, if required & mention them clearly.
4. Draw neat sketches wherever necessary.

Q.1 Do as directed.

[12]

- (a) "The NAND and NOR operators are distributive" State T/F with justification. **[2]**
- (b) Differentiate I^2L and RTL logic family. **[2]**
- (c) What are the weights of the MSB of **[1]**
 - (i) 10-bit binary number and
 - (ii) 8-bit hex number?
- (d) How does a priority encoder differ from an ordinary encoder? **[1]**
- (e) What is the difference between serial and parallel transfer? What type of register is used in each case? **[2]**
- (f) Construct a mod 07-counter using MSI circuit. Give two alternatives. **[2]**
- (g) Find the complement of $F = x(y'z' + yz)$ **[2]**

Q.2 Attempt following questions.

[12]

- (a) Design a combinational circuit with four input lines that represent a decimal digit in BCD and four output lines that generate 9's complement of the input digit. **[6]**
- (b) Derive the state equations for the sequential circuit using state table given below. List the don't care terms. **[6]**

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
ABC	ABC	ABC	Y	Y
001	001	010	0	0
010	011	100	0	0
011	001	100	0	0
100	101	100	0	1
101	001	100	0	1

Q.3 Attempt following questions

[12]

- (a) Differentiate PLA and ROM. **[2]**
- (b) Design the sequential circuit described by the following state equations. Use JK flip-flops. **[4]**
$$A(t+1) = A'Bx' + AB'x' + ABx' + ABx$$
$$B(t+1) = A'x + A'B + xB$$
- (c) Simplify the following Boolean function by means of Tabulation method. **[6]**
$$F(w,x,y,z) = \Pi(0,1,2,3,4,10,11)$$