



DHARMSINH DESAI UNIVERSITY, NADIAD
FACULTY OF TECHNOLOGY
B.TECH - IT - Semester - III
SUBJECT: (IT 301) Design of Digital Circuits

Examination : Block Exam
Date : 18/10/2014
Time : 11:00 to 12:15

Seat No. :
Day : Saturday
Max. Marks : 36

INSTRUCTIONS:

1. Figures to the right indicate maximum marks for that question.
2. The symbols used carry their usual meanings.
3. Assume suitable data, if required & mention them clearly.
4. Draw neat sketches wherever necessary.

Q.1 Do as directed. [12]

- (a) Represent the Decimal number, 620 in [2]
i) BCD Code ii) Excess-3 Code iii) 2421 Code iv) Binary
- (b) Find complement of: $F = X(Y'Z' + YZ)$ [2]
- (c) State T/F with Justification: "The NAND operator is Associative" [2]
- (d) Why Flip-Flop is called a single-bit register? [2]
- (e) How do the look-ahead carry adder speed up the addition process? [2]
- (f) Obtain Gray Code for decimal 12 and decimal 15. [2]

Q.2 Attempt following questions. [12]

- (a) Determine the Prime Implicants of the function: [6]
 $F(A,B,C,D) = \sum (0,4,6,7,8,9,10,11,15)$
- (b) Design the sequential Circuit using JK Flip-Flop for given State Stable [6]

Present State		Next State			
		X=0		X=1	
A	B	A	B	A	B
0	0	0	0	0	1
0	1	1	0	0	1
1	0	1	0	1	1
1	1	1	1	0	0

Q.3 Attempt following questions [12]

- (a) Signal A,B,C,D and D' are available. Using a single 8 x 1 Mux and no other gate implement the Boolean function. [6]
 $F = \sum (0,1,3,4,8,9,15)$
- (b) Derive PLA program table for full subtractor. [6]