



DHARMSINH DESAI UNIVERSITY, NADIAD
FACULTY OF TECHNOLOGY
B.TECH - IT - Semester - III
SUBJECT: (IT 301) Design of Digital Circuits

Examination : First Sessional
Date : 04/08/2016
Time : 9:30 to 10:45

Seat No. :
Day : Thursday
Max. Marks : 36

INSTRUCTIONS:

1. Figures to the right indicate maximum marks for that question.
2. The symbols used carry their usual meanings.
3. Assume suitable data, if required & mention them clearly.
4. Draw neat sketches wherever necessary.

Q.1 Do as directed. [12]

- (a) Simplify the following Boolean expressions(Use Boolean algebra): [3]
- i) $wx'y + x + xz' + wxz' + w'y$
 - ii) $p'q'r + (p + q + r')' + p'q'r's$
- (b) Encode the decimal digits 0,1,29 for weighted code 4221 so that 9's complement of each decimal digit is obtained by changing 1's to 0's and 0's to 1's. [2]
- (c) Express the functions in sum of minterms and product of maxterms. [2]
- i) $F(x,y,z) = 1$
 - ii) $F(p,q,r) = (pq + r)(q + pr)$
- (d) Perform the subtraction for the following decimal number using 10's complement and 9's complement. i) $(635.7) - (419.8)$ [2]
- (e) Convert the number $(724.5)_{10}$ into following codes: [3]
- i) Base 4
 - ii) Base 6
 - iii) Base 11

Q.2 Attempt following questions. [12]

- (a) Simplify the given function using Tabulation method: [7]
 $F(A,B,C,D,E,F) = \sum(1,2,5,6,9,18,19,25,28,41,45,57,59,61)$
- (b) Design and implement the Full-Subtractor circuit. (represent 2 variation of it) [5]
- OR**
- (b) Implement the function $F = (x' + z')(w' + y' + z)(w + x' + y' + z)(w' + x + y' + z')$ with the following two level forms: [5]
- i) NOR-OR
 - ii) NAND-AND

Q.3 Attempt following questions [12]

- (a) Show that dual of Ex-OR is equal to its complement. [2]
- (b) Determine the even-parity bit generated when the message consist of ten decimal digits in 2421 code. [4]
- (c) Simplify the given Boolean function F using don't care condition d, in SOP and POS from: [6]
 $F = \sum(0,2,6,9,11,13,15,20,25,31)$
 $D = \sum(4,16,18,22,27,29)$

OR

Q.3 Attempt following questions [12]

- (a) State and Prove Absorption Theorem. [2]
- (b) Given the function $F = ABC + A'B'C' + AB'C + A'BC'$. [4]
Implement only using following gates.
 - i) OR & NOT gate.
 - ii) AND & NOT gate.
- (c) Simplify the following Boolean function using K-map & implement them using universal logical gates (2 level NAND & 2 level NOR): [6]
 $F(W,X,Y,Z) = \sum(5,6,7,9,10,11,13,14,15)$